

HW4


$$\begin{aligned} 1. \quad U_{th} &= U \times \frac{R_1}{R_1 + R_2} \\ &= 60 \times \frac{40}{40 + 10} \\ &= 48V \end{aligned}$$

$$R_{1,2} = \frac{1}{\frac{1}{40} + \frac{1}{8}} = \frac{20}{3}$$

$$U_{12} = U \times \frac{\frac{20}{3}}{10 + \frac{20}{3}} = 24V$$

$$I = \frac{U}{R} = \frac{24V}{8\Omega} = 3A$$
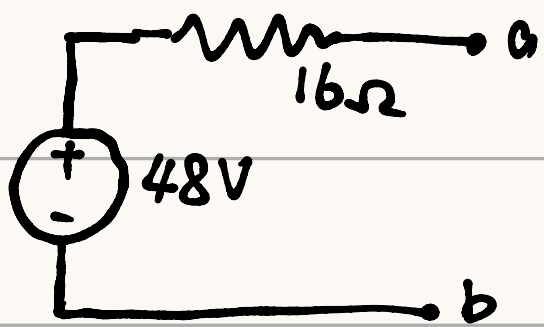
$$R_{th} = \frac{U_{th}}{I} = \frac{48V}{3A} = 16\Omega$$



$$2.(a) \quad I = \frac{U}{R} = \frac{45V}{6 + R_0}$$

$$P = I^2 \cdot R = \frac{6 \times 45^2}{(6 + R_0)^2} =$$

$$\text{when } R_0 = 0 \quad P_{max} = 337.5W$$

$$(b) \quad P_{max} = 337.5W$$