

ECE/CoE 0101 – Linear Circuits and Systems

Laboratory # 5 – Power Transfer in Circuits

Objectives:

- Understand how to calculate Thevenin equivalent circuits
- Demonstrate that maximum power transfer is achieved for a given circuit when the load resistance is equivalent to the Thevenin resistance.

Introduction

This laboratory session builds upon the concepts demonstrated in Lab 3 on Thevenin's theorem. In that Lab you learned how the circuit shown in Figure 1, below, could be transformed into a Thevenin equivalent circuit as shown in Figure 2, below (R_T has a different value than that used in Lab 3). Here in Lab 4, we'll see how a Thevenin network, can be used as an equivalent model for the source circuit and how it interacts with a resistive load to deliver the maximum power to the load.

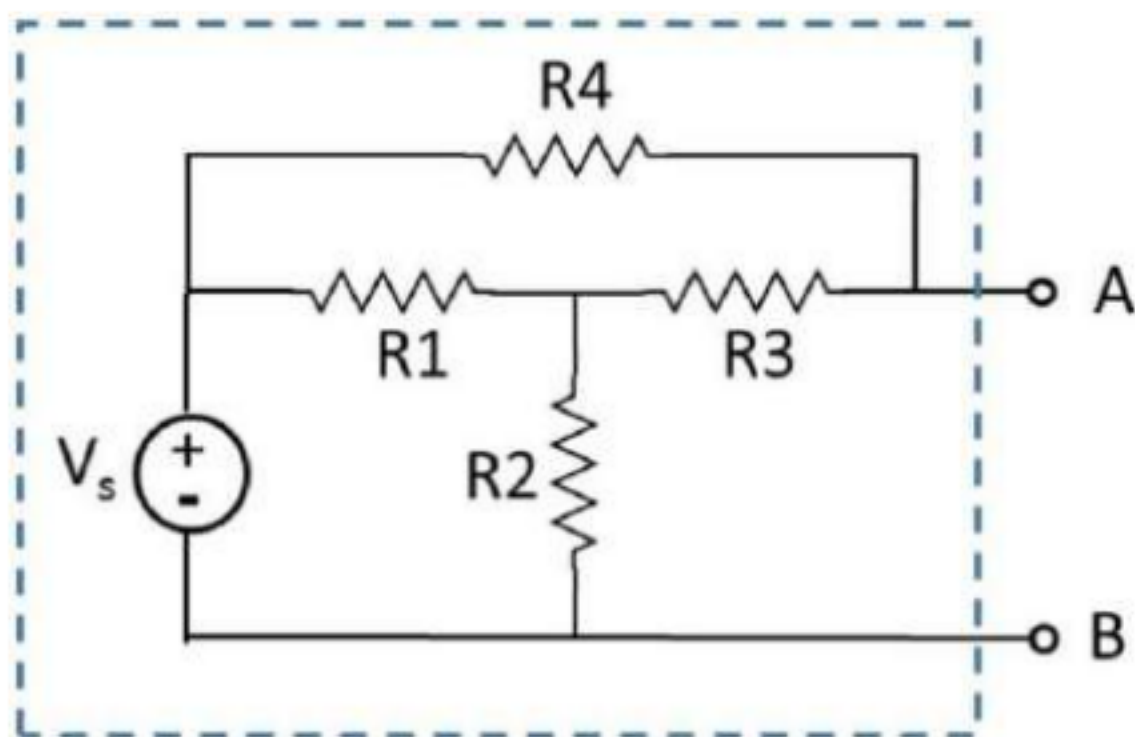


Figure 1 - Source circuit with the following given component values: $V_s = 5V$, $R_1 = 600\ \Omega$, $R_2 = 1.2\ k\Omega$, $R_3 = 1.8\ k\Omega$, $R_4 = 3.9\ k\Omega$.

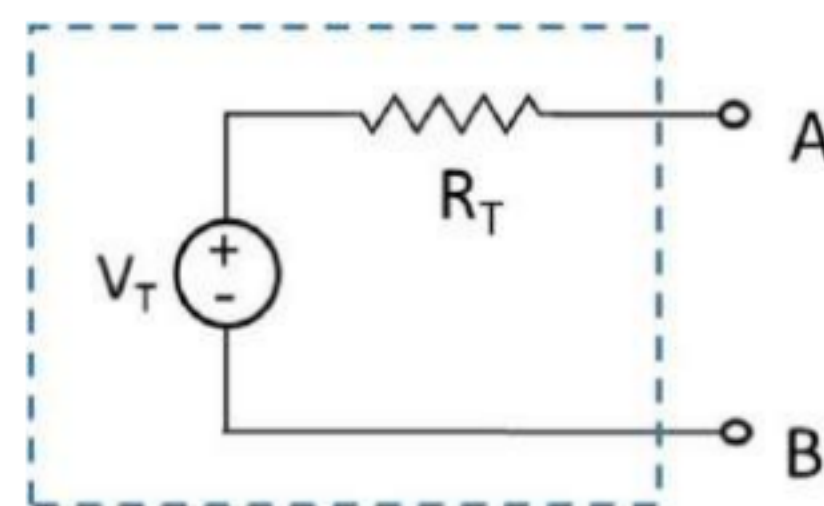


Figure 2 - Thevenin equivalent circuit.

This lab's objective is to determine the necessary source conditions to deliver maximum power to a known specified load. Specifically, we want to determine R_X such that the source circuit will deliver the maximum power to the load resistor R_L of specified resistance (here $R_T = 2.2\ k\Omega$). The specific circuit of interest is

Figure 3, below, with the power source being the entire circuit within the dotted line box left of terminals A and B.


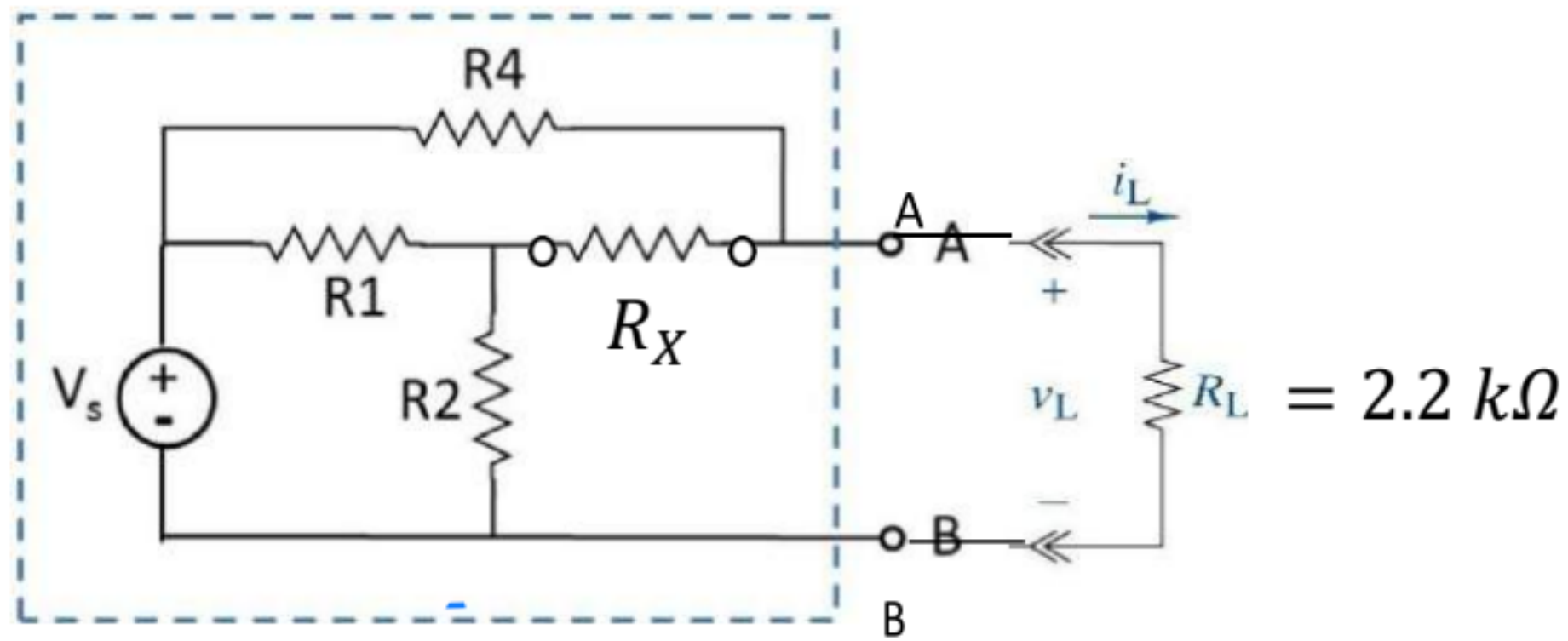


Figure 3 - Source circuit (left of terminals) and load resistor (right of terminals A-B) for homework analysis and lab measurement. Use the values for V_s , R_1 , R_2 , and R_4 given in Fig. 1.

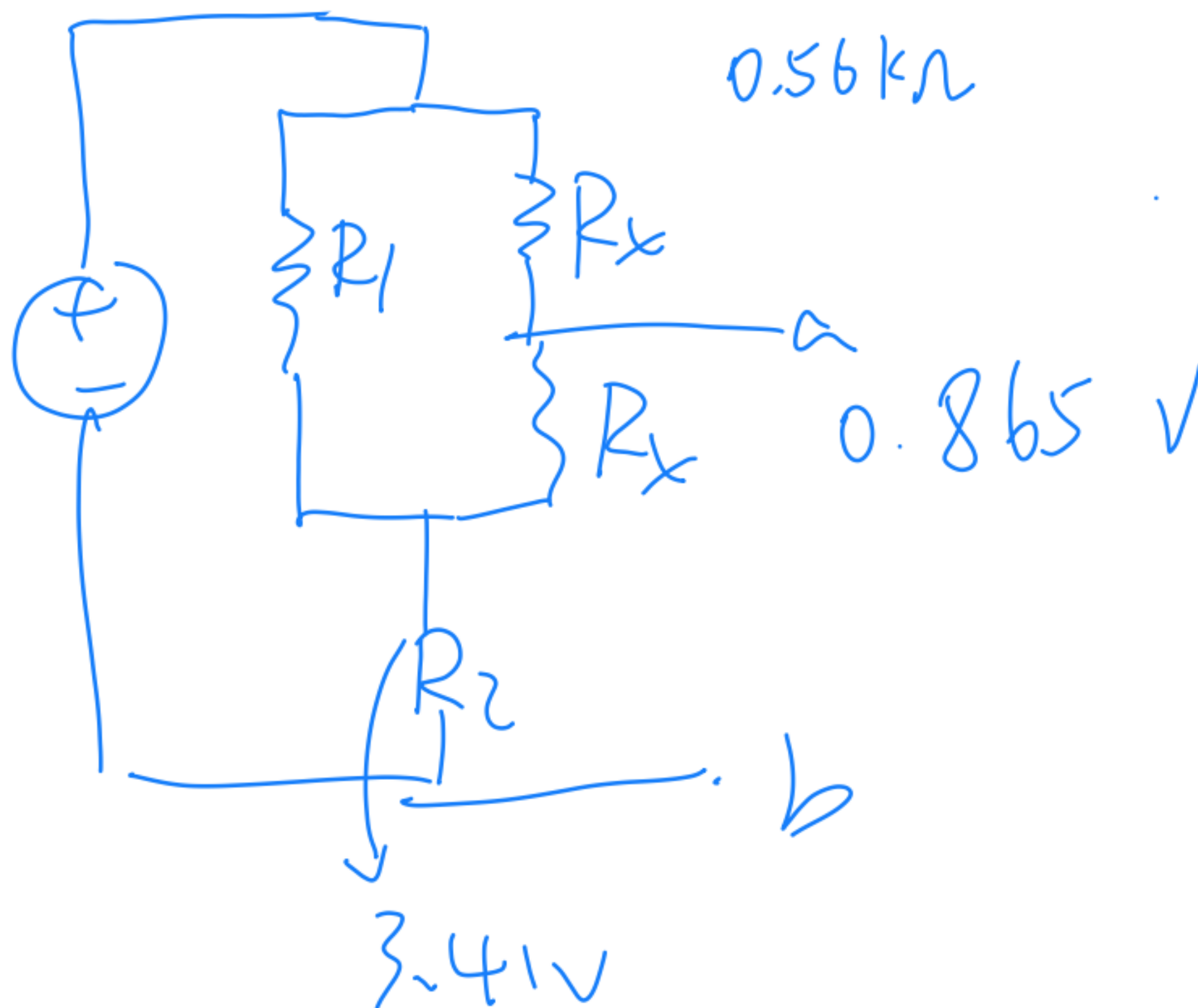

Homework

Name 刘德熙 张鹤扬

(30 points) Knowing now (after Lab No. 3) how to calculate the equivalent Thevenin circuit for a source, use this to calculate the value of resistor R_X that will enable the source circuit (all left of terminals A & B) to deliver the maximum power to the $2.2 \text{ k}\Omega$ load resistor R_L (right of terminals A & B). Also calculate the value for V_T . Then calculate the maximum power transfer expected, p_{\max} . Neatly show your calculation and the resultant values for R_X , V_T , and P_{\max} in the following space:

$$R_L = (R_1 || R_2 + R_X) || R_4 = 2.2 \text{ k}\Omega$$

$$\frac{(0.4 + R_X)3.9}{0.4 + R_X + 3.9} = 2.2 \Rightarrow R_X = 4.647 \text{ k}\Omega$$

$$R_{14X} = R_1 || (R_4 + R_X) = \frac{0.6 \times (3.9 + 4.647)}{0.6 + 3.9 + 4.647} = 0.56 \text{ k}\Omega$$

$$R_{eq} = R_{14X} + R_2 = 1.76 \text{ k}\Omega$$

$$I = \frac{V}{R_{eq}} = \frac{5 \text{ V}}{1.76 \text{ k}\Omega} = 2.841 \times 10^{-3} \text{ A}$$

$$V_T = I \cdot R_2 + I \cdot R_{14X} \cdot \frac{R_X}{R_X + R_4} = 3.41 \text{ V} + 2.841 \times 10^{-3} \text{ A} \times 0.56 \text{ k}\Omega \times \frac{4.647}{4.647 + 3.9} = 4.275 \text{ V}$$

$$P_{\max} = \frac{V_T^2}{4R_X} = 2.077 \times 10^{-3} \text{ W}$$

$$R_X = \underline{4.647 \text{ k}\Omega}$$

$$V_T = \underline{4.275 \text{ V}}$$

$$P_{\max} = \underline{2.077 \times 10^{-3} \text{ W}}$$

Laboratory Procedure

1. Build the circuit shown in Figure 3 using the value for R_X that you determined above.
2. Measure the following operating parameters in the assembled circuit:

a. (6 points) Maximum open circuit source voltage at terminals AB $V_{OC} = 4.277V$

b. (6 points) Max. short circuit source current between terminals AB $I_{RL} = 1.935mA$

c. (18 points) Actual power delivered to the 2.2 k Ω load resistor (i.e. $P = VI$ for this resistor).

V_{RL} (measured) = $2.133V$

I_{RL} (measured) = $0.970mA$

P_{RL} (calculated from measurements) $2.069 \times 10^{-3}W$

3. (10 points) Calculate the maximum power transfer expected from 2a and 2b – see the following equation. Compare this with the power measured/calculated in 2c.

$$p_{max} = \frac{(V_T)^2}{4R_T} = \left(\frac{V_T}{2}\right)\left(\frac{V_T}{2R_T}\right) = \left(\frac{V_{oc}}{2}\right)\left(\frac{I_{sc}}{2}\right) = 2.068 \times 10^{-3}W$$

Comments on Comparison:

The difference between P_{RL} and P_{max} less than 0.1%, and it is acceptable, two results are identical.

4. (15 points) Replace R_X with resistors of the following values: 680 Ω , 5.6k Ω . Re-measure the power delivered to R_L for each condition. For each data point, calculate the ratios $\frac{R_L}{R_T}$ and $\frac{P}{P_{max}}$.

$$R_L = \frac{(0.4 + R_X) \times 3.9}{4.3 + R_X}$$

680 Ω

$$V = 2.67V$$

$$I = 1.215mA$$

$$\frac{R_L}{R_T} = \frac{2200}{846} = 2.6$$

$$\frac{P}{P_{max}} = 1.568$$

5.6k Ω

$$V = 2.09V$$

$$I = 0.950mA$$

$$\frac{R_L}{R_T} = \frac{2200}{2364} = 0.93$$

$$\frac{P}{P_{max}} = 0.96$$

5. (15 points) Plot your measured results from Q4 on the semi-log graph given below. Are your measurements consistent with the expected theoretical graph?

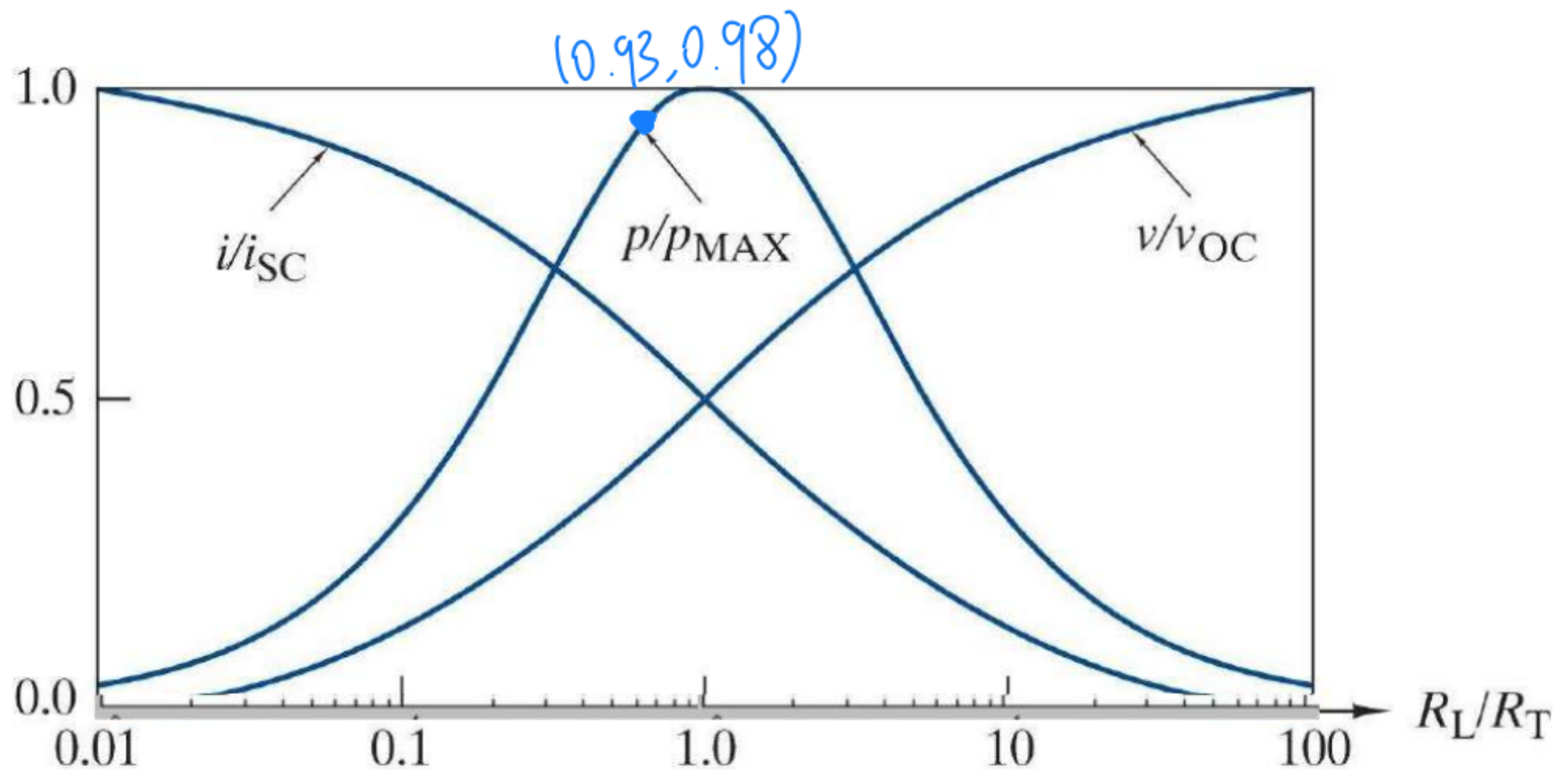


Figure 3-58
© John Wiley & Sons, Inc. All rights reserved.

- ① $R_x = 5.6 k\Omega$ measurements consistent with the expected theoretical graph
- ② $R_x = 680 \Omega$, it isn't consistent with the expected theoretical graph

Blank lined paper for writing.

Blank lined paper for writing.