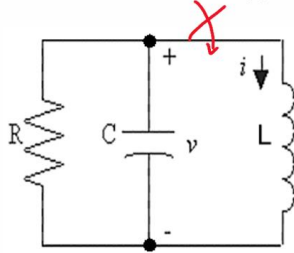


Initial conditions-2

Example: Consider the parallel RLC circuit with $R = 604 \text{ m}\Omega$, $L = 20 \text{ mH}$ and $C = 207 \text{ mF}$

Note that these values are approximate, but come close to giving the correct values for $s = -4 \pm j15$



$$s = -4 \pm j15$$

$$i_n = e^{-4t} (B_1 \cos 15t + B_2 \sin 15t)$$

$$i(0) = 0 \text{ A}$$

$$v(0) = 30 \text{ V}$$

We want to find the values of B_1 and B_2 . Let's apply the first initial condition by evaluating i_n from the solution form and equating this to the value of the initial condition (IC):

$$i_n(0) = e^{-4 \cdot 0} (B_1 \cos 15 \cdot 0 + B_2 \sin 15 \cdot 0) = 0$$

$$1 \cdot (B_1 \cdot 1 + B_2 \cdot 0) = 0$$

$$B_1 = 0$$

Good, that gets rid of half the solution. But, how to use $v(0)$? Well

Find B_2 ?

Initial conditions-3


$$v = L \frac{di}{dt} \quad \text{so} \quad \frac{di}{dt}(0) = \frac{v(0)}{L} = \frac{30 \text{ V}}{20 \text{ mH}} = 1500 \text{ A/s}$$


To get $\frac{di}{dt}(0)$ from the solution form, we have to differentiate it. It's a good thing B_1 was zero, it makes the differentiation half the effort.

$$\frac{di_n}{dt} = \frac{d}{dt} e^{-4t} (B_2 \sin 15t) = -4e^{-4t} (B_2 \sin 15t) + e^{-4t} (15 \cdot B_2 \cos 15t)$$

$$\frac{di_n}{dt}(0) = -4 \cdot 1 \cdot (B_2 \cdot 0) + 1 \cdot (15 \cdot B_2 \cdot 1) = 1500$$
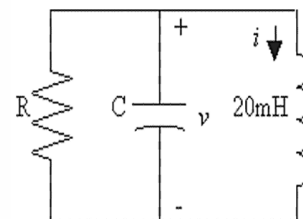
$$B_2 = \frac{1500}{15} = 100 \quad \text{and} \quad i_n = 100e^{-4t} \sin 15t$$



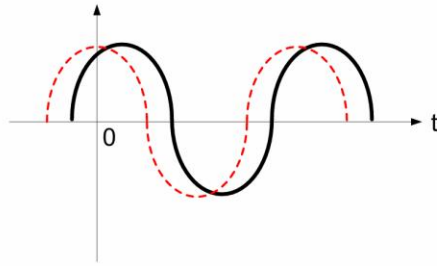

$$-V_m \cos(\omega t)$$

$$-V_m \cos(\omega t + \phi)$$


ϕ : phase advance

move waveform to the left

ϕ is the phase angle of the waveform and its reference
to where the waveform begins


SOURCE TRANSFORMATION AND THEVENIN-NORTON EQUIVALENT CIRCUIT

Example:

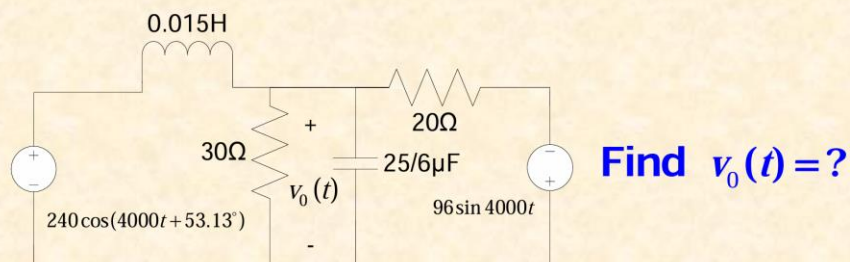

左右两个部分分别使用戴维南等效，再分析节点的电流，使用基尔霍夫定律

Example:

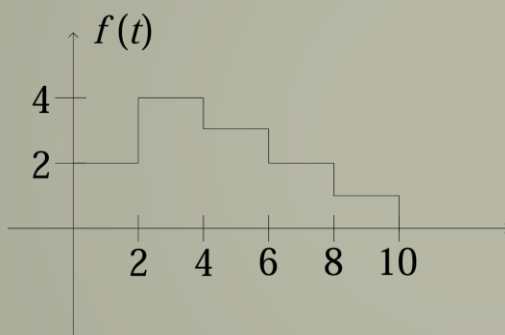

more complex functions
can be decomposed into a
series (sum) of unit step

$$f(t) = 2u(t) + 2u(t-2) - u(t-4) \\ - u(t-6) - u(t-8) - u(t-10)$$

Laplace Transform /Operational Transform

Integration:

Using integral by parts $\int u dv = uv - \int v du$

$$\mathcal{L}\left\{\int_{0^-}^t f(x) dx\right\} = \int_{0^-}^{\infty} \left[\int_{0^-}^t f(x) dx\right] e^{-st} dt$$

We can do it by integration by parts or using Laplace

Transform Derivative results.

$$u = \int_{0^-}^t f(x) dx; dv = e^{-st} dt; du = f(t) dt; v = -\frac{e^{-st}}{s} \Big|_{0^-}^{\infty}$$


w.r. to time, t $\left[-\frac{e^{-st}}{s} \int_{0^-}^t f(x) dx \right] + \int_{0^-}^{\infty} \frac{e^{-st}}{s} f(t) dt = 0 + \frac{F(s)}{s} = \frac{F(s)}{s}$

Alternate proof: $L\left\{\int_{0^-}^t f(x) dx\right\} = L\{g(t)\}; \frac{dg}{dt} = f(t); g(0) = 0$


$$L\left\{\frac{d}{dt} f(t)\right\} = sF(s) - f(0^-) \quad L\left\{\frac{dg}{dt}\right\} = L\{f(t)\}; sG(s) = F(s); G(s) = \frac{F(s)}{s}$$

$$G(s) = L\left\{\int_{0^-}^t f(x) dx\right\} = \frac{F(s)}{s}$$

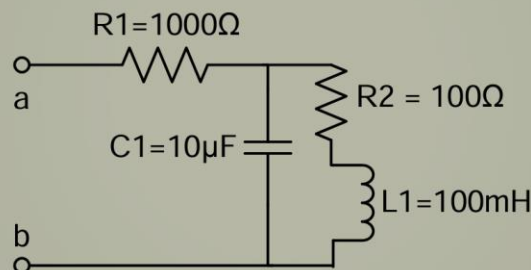- find Z_{ab}
- Find poles and zeros of Z_{ab}



- find Z_{ab}

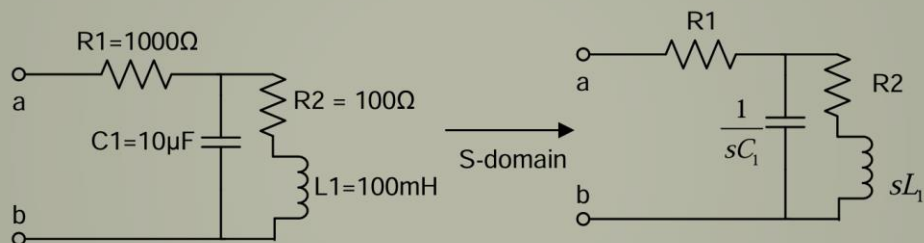

$$Z_2 = \frac{1}{sC_1} \parallel (R_2 + sL_1) = \frac{\frac{1}{sC_1} \times (R_2 + sL_1)}{\frac{1}{sC_1} + R_2 + sL_1}$$

$$= \frac{R_2 + sL_1}{s^2 L_1 C_1 + s R_2 C_1 + 1}$$

1. 它们之间的数学关系


在拉普拉斯变换中，变量 s 是一个复数，通常写成：

$$s = \sigma + j\omega$$


其中 σ 代表衰减指数，而 $j\omega$ 代表角频率。

- 当你学 $X_C = \frac{1}{j\omega C}$ 时：你研究的是**正弦稳态**。这时候假设电路已经通电很久了，波形是稳定的正弦波，没有衰减（即 $\sigma = 0$ ）。此时 s 直接变成了 $j\omega$ 。
- 当你学 $Z_C = \frac{1}{sC}$ 时：你研究的是**全响应**。它不仅包括了稳态，还包括了开关合上那一刻的暂态（瞬态）过程（即 $\sigma \neq 0$ 的部分）。

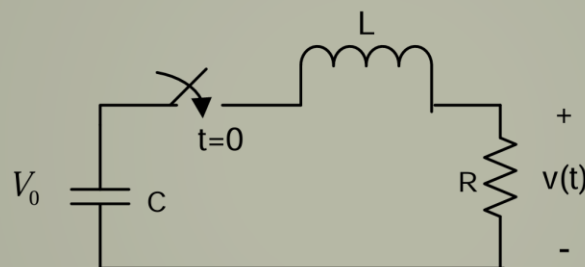● C is initially charged to a voltage of V_0



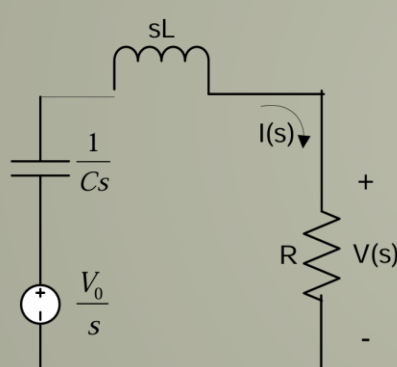Laplace transform of the circuit for $t > 0$



$$\frac{V_0}{s} = I(s) \left(\frac{1}{sC} + R + sL \right)$$

So that

$$I(s) = \frac{\frac{V_0}{s}}{R + sL + \frac{1}{sC}} = \frac{CV_0}{s^2 LC + RCs + 1} = \frac{\frac{V_0}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

and

$$V(s) = RI(s) = \frac{R \frac{V_0}{L}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

Next to take the inverse transform

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0 = s^2 + 2\alpha s + \omega_0^2$$

$$\omega_0 = \text{resonant radian frequency} = \sqrt{\frac{1}{LC}}$$

$$\alpha = \text{Neper frequency} = \frac{R}{2L}$$

The poles will be the roots of the denominator polynomial

$$s^2 = \frac{-2\alpha \pm \sqrt{4\alpha^2 - 4\omega_0^2}}{2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -P_1; -P_2$$

Depending upon the values of α and ω_0 have 3 cases to consider:

(1) If $\alpha^2 > \omega_0^2 (R^2 > \frac{4L}{C})$ (over damped)

$$-P_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}; -P_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2} \quad (2 \text{ real distinct roots})$$

(2) If $\alpha^2 = \omega_0^2 (R^2 = \frac{4L}{C})$ (critical damped)

$$-P_1 = -P_2 = -\alpha \quad (2 \text{ real repeated roots})$$

(3) If $\alpha^2 < \omega_0^2 (R^2 < \frac{4L}{C})$ (under damped)

$$-P_1 = -\alpha + j\beta; -P_2 = -\alpha - j\beta$$

$$\text{where } \beta = \sqrt{\omega_0^2 - \alpha^2} \quad (2 \text{ complex conjugate roots})$$

Case 1: Over Damped

$$\text{Poles are } -P_1 = -\alpha + \sqrt{\alpha^2 - \omega_0^2}; -P_2 = -\alpha - \sqrt{\alpha^2 - \omega_0^2}$$

$$V(s) = \frac{\frac{R}{L}V_0}{s^2 + \frac{R}{L}s + \frac{1}{LC}} = \frac{\frac{R}{L}V_0}{(s+P_1)(s+P_2)}$$


Perform a partial fraction expansion

$$V(s) = \frac{\frac{1}{2\sqrt{\alpha^2 - \omega_0^2}} \frac{R}{L} V_0}{s + \alpha - \sqrt{\alpha^2 - \omega_0^2}} + \frac{\frac{-1}{2\sqrt{\alpha^2 - \omega_0^2}} \frac{R}{L} V_0}{s + \alpha + \sqrt{\alpha^2 - \omega_0^2}}$$

Case 1: Over Damped

The time-domain response
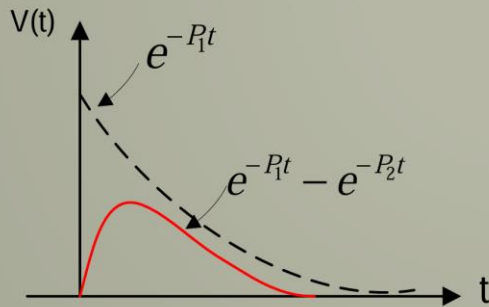
$$v(t) = \frac{R}{2L} V_0 \frac{1}{\sqrt{\alpha^2 - \omega_0^2}} (e^{-(\alpha - \sqrt{\alpha^2 - \omega_0^2})t} - e^{-(\alpha + \sqrt{\alpha^2 - \omega_0^2})t}) u(t)$$



$P_1 < P_2$; so

$e^{-P_2 t}$ decay faster than $e^{-P_1 t}$

$$v(t) = \frac{V_0 \alpha}{\sqrt{\alpha^2 - \omega_0^2}} (e^{-P_1 t} - e^{-P_2 t}) u(t)$$


P_1 falling time constant

P_2 rising time constant

Case 2: Critically Damped

Poles are $-P_1 = -P_2 = -\alpha$

$$V(s) = \frac{\frac{R}{L} V_0}{(\alpha + s)^2} \quad v(t) = (A + Bt) e^{-\alpha t} u(t) \quad \text{Where } A=1 \quad B = \frac{R}{L} V_0$$

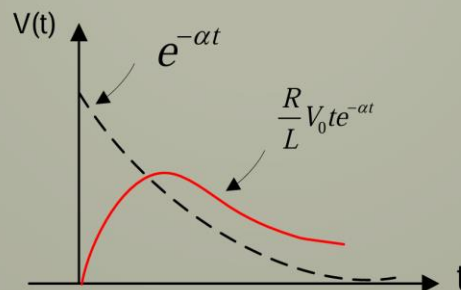

Case 3: Under Damped

The inverse Laplace transform of this is:

$$v(t) = V_0 \frac{\alpha}{\beta} \frac{1}{j} [e^{-\alpha t} e^{j\beta t} - e^{-\alpha t} e^{-j\beta t}] u(t)$$


or using

$$\sin \beta t = \frac{e^{j\beta t} - e^{-j\beta t}}{2j}$$



$$v(t) = V_0 \frac{2\alpha}{\beta} e^{-\alpha t} \sin(\beta t) u(t)$$

$$v(t) = V(s) = \frac{\frac{R}{L} V_0}{(s + \alpha - j\beta)(s + \alpha + j\beta)}$$

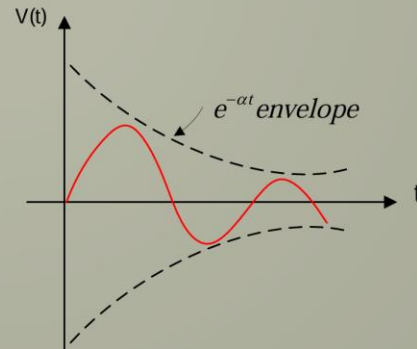
$$V(s) = \frac{\frac{1}{j2\beta} \frac{R}{L} V_0}{(s + \alpha - j\beta)} + \frac{\frac{-1}{j2\beta} \frac{R}{L} V_0}{(s + \alpha + j\beta)}$$



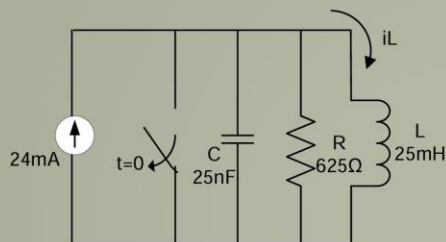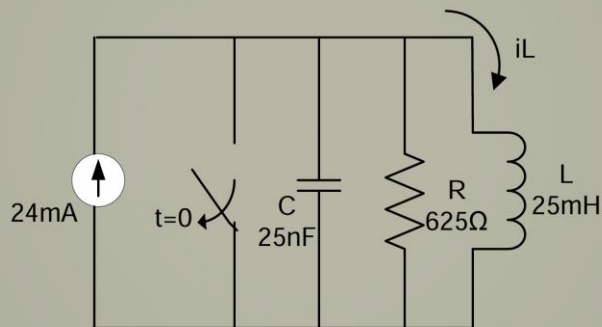- The step response of a parallel circuit
- Find: $i_L(t)$



S-domain

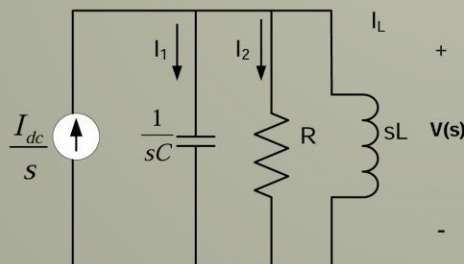

$$I_L = \frac{V(s)}{sL}$$

$$\frac{I_{dc}}{s} = I_1 + I_2 + I_L = \frac{V(s)}{1/sC} + \frac{V(s)}{R} + \frac{V(s)}{sL}$$

$$V(s) = \frac{\frac{I_{dc}}{C}}{s^2 + (\frac{1}{RC})s + \frac{1}{LC}}$$

$$I_L = V(s) \frac{1}{sL} = \frac{\frac{I_{dc}}{LC}}{s(s^2 + (\frac{1}{RC})s + \frac{1}{LC})}$$

- The step response of a parallel circuit

$$I_L = V(s) \frac{1}{sL} = \frac{\frac{I_{dc}}{LC}}{s(s^2 + (\frac{1}{RC})s + \frac{1}{LC})}$$

Substituting the numerical values of R, C, L, I_{dc}

$$I_L = \frac{384 \times 10^5}{s(s^2 + 64000s + 16 \times 10^8)}$$

$$\text{Roots: } s = 0; s = -32000 \pm j24000$$

$$I_L = \frac{384 \times 10^5}{s(s + 32000 - j24000)(s + 32000 + j24000)}$$

- The step response of a parallel circuit

Perform a partial fraction expansion

$$I_L = \frac{k_1}{s} + \frac{k_2}{s + 32000 + j24000} + \frac{k_2^*}{s + 32000 - j24000}$$

$$k_1 = 24 \times 10^{-3}; k_2 = 20 \times 10^{-3} \angle 126.87^\circ$$


$$i_L = [24 + 40e^{-32000t} \cos(24000t + 126.87^\circ)]u(t) \text{ mA}$$

Check Final value of $I_L; t \rightarrow \infty$ the inductor will
be short circuit $I_L = 24 \text{ mA} (\lim_{s \rightarrow 0}) \quad i(t \rightarrow \infty) = 24 \text{ mA}$

6.13 Initially there was no energy stored in the 5 H inductor in the circuit in Fig. P6.13 when it was placed across the terminals of the voltmeter. At

$t = 0$ the inductor was switched instantaneously to position b where it remained for 1.6 s before returning instantaneously to position a. The d'Arsonval voltmeter has a full-scale reading of 20 V and a sensitivity of $1000 \Omega/\text{V}$. What will the reading of the voltmeter be at the instant the switch returns to position a if the inertia of the d'Arsonval movement is negligible?

Figure P6.13

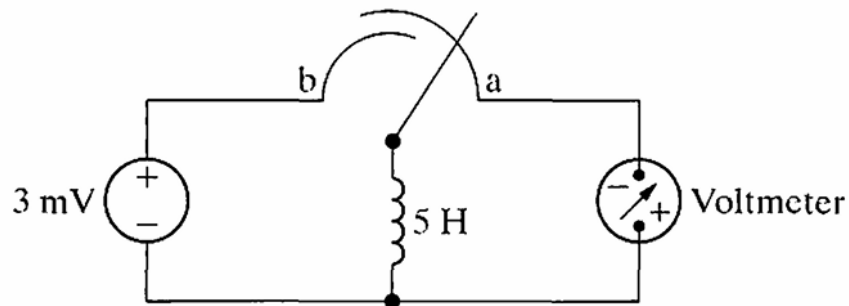

P 6.13 For $0 \leq t \leq 1.6 \text{ s}$:

$$i_L = \frac{1}{5} \int_0^t 3 \times 10^{-3} dx + 0 = 0.6 \times 10^{-3} t$$

$$i_L(1.6 \text{ s}) = (0.6 \times 10^{-3})(1.6) = 0.96 \text{ mA}$$

$$R_m = (20)(1000) = 20 \text{ k}\Omega$$

$$v_m(1.6 \text{ s}) = (0.96 \times 10^{-3})(20 \times 10^3) = 19.2 \text{ V}$$


6.23 The three inductors in the circuit in Fig. P6.23 are connected across the terminals of a black box at $t = 0$. The resulting voltage for $t > 0$ is known to be

$$v_o = 2000e^{-100t} \text{ V.}$$

If $i_1(0) = -6 \text{ A}$ and $i_2(0) = 1 \text{ A}$, find


- $i_o(0)$;
- $i_o(t), t \geq 0$;
- $i_1(t), t \geq 0$;
- $i_2(t), t \geq 0$;
- the initial energy stored in the three inductors;
- the total energy delivered to the black box; and
- the energy trapped in the ideal inductors.

Figure P6.23

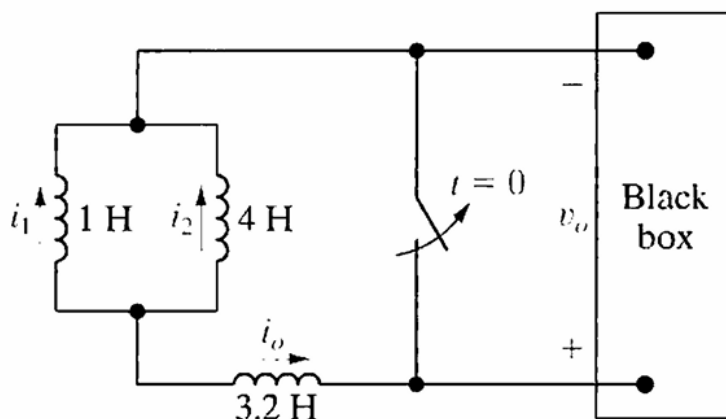


P 6.23 [a] $i_o(0) = -i_1(0) - i_2(0) = 6 - 1 = 5 \text{ A}$

[b]

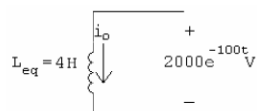

$$\begin{aligned} i_o &= -\frac{1}{4} \int_0^t 2000e^{-100x} dx + 5 = -500 \left. \frac{e^{-100x}}{-100} \right|_0^t + 5 \\ &= 5(e^{-100t} - 1) + 5 = 5e^{-100t} \text{ A,} \quad t \geq 0 \end{aligned}$$

[c]

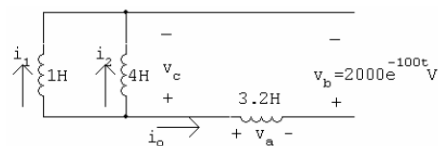

$$v_a = 3.2(-500e^{-100t}) = -1600e^{-100t} \text{ V}$$

$$\begin{aligned} v_c &= v_a + v_b = -1600e^{-100t} + 2000e^{-100t} \\ &= 400e^{-100t} \text{ V} \end{aligned}$$

$$i_1 = \frac{1}{1} \int_0^t 400e^{-100x} dx - 6$$

$$= -4e^{-100t} + 4 - 6$$

$$i_1 = -4e^{-100t} - 2 \text{ A} \quad t \geq 0$$

$$[\text{d}] \quad i_2 = \frac{1}{4} \int_0^t 400e^{-100x} dx + 1$$

$$= -e^{-100t} + 2 \text{ A}, \quad t \geq 0$$

$$[\text{e}] \quad w(0) = \frac{1}{2}(1)(6)^2 + \frac{1}{2}(4)(1)^2 + \frac{1}{2}(3.2)(5)^2 = 60 \text{ J}$$

$$[\text{f}] \quad w_{\text{del}} = \frac{1}{2}(4)(5)^2 = 50 \text{ J}$$

$$[\text{g}] \quad w_{\text{trapped}} = 60 - 50 = 10 \text{ J}$$

$$\text{or} \quad w_{\text{trapped}} = \frac{1}{2}(1)(2)^2 + \frac{1}{2}(4)(2)^2 + 10 \text{ J (check)}$$

计算电感的能量的时候，必须要分开独立计算。

常规的理解方式，可以先计算出初始的能量，然后计算出最终的能量，传递的能量通过二者相减得到

可以通过等效的元素，得出传递的能量


先通过等效元件，得出总的电流，在对每一个小的元件进行积分，得到对应的电流

6.35 At $t = 0$, a series-connected capacitor and inductor are placed across the terminals of a black box, as shown in Fig. P6.35. For $t > 0$, it is known that

$$i_o = 1.5e^{-16,000t} - 0.5e^{-4000t} \text{ A.}$$

If $v_c(0) = -50 \text{ V}$ find v_o for $t \geq 0$.

Figure P6.35

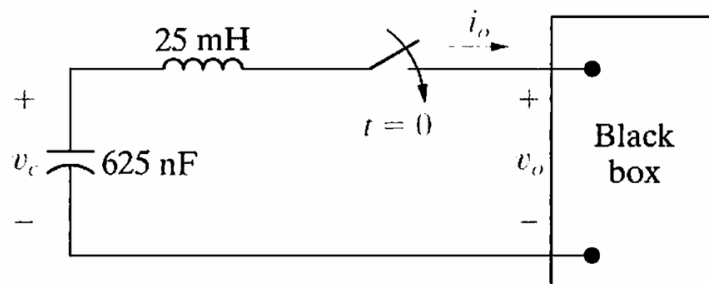

$$\begin{aligned}
\text{P 6.35} \quad v_c &= -\frac{1}{0.625 \times 10^{-6}} \left(\int_0^t 1.5e^{-16,000x} dx - \int_0^t 0.5e^{-4000x} dx \right) - 50 \\
&= 150(e^{-16,000t} - 1) - 200(e^{-4000t} - 1) - 50 \\
&= 150e^{-16,000t} - 200e^{-4000t} \text{ V} \\
v_L &= 25 \times 10^{-3} \frac{di_o}{dt} \\
&= 25 \times 10^{-3} (-24,000e^{-16,000t} + 2000e^{-4000t}) \\
&= -600e^{-16,000t} + 50e^{-4000t} \text{ V} \\
v_o &= v_c - v_L \\
&= (150e^{-16,000t} - 200e^{-4000t}) - (-600e^{-16,000t} + 50e^{-4000t}) \\
&= 750e^{-16,000t} - 250e^{-4000t} \text{ V}, t > 0
\end{aligned}$$


注意电感和电容的符号，可以通过楞次定律检查符号

7.3 The switch in the circuit in Fig. P7.3 has been open for a long time. At $t = 0$ the switch is closed.

PSPICE
MULTISIM

- Determine $i_o(0^+)$ and $i_o(\infty)$.
- Determine $i_o(t)$ for $t \geq 0^+$.
- How many milliseconds after the switch has been closed will the current in the switch equal 3 A?

Figure P7.3

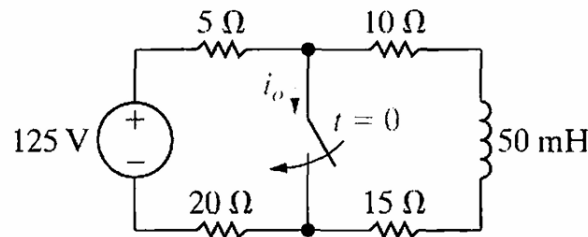

$$\begin{aligned}
\text{P 7.3} \quad [\text{a}] \quad i_L(0) &= \frac{125}{50} = 2.5 \text{ A} \\
i_o(0^+) &= \frac{125}{25} - 2.5 = 5 - 2.5 = 2.5 \text{ A} \\
i_o(\infty) &= \frac{125}{25} = 5 \text{ A} \\
[\text{b}] \quad i_L &= 2.5e^{-t/\tau}; \quad \tau = \frac{L}{R} = \frac{50 \times 10^{-3}}{25} = 2 \text{ ms} \\
i_L &= 2.5e^{-500t} \text{ A} \\
i_o &= 5 - i_L = 5 - 2.5e^{-500t} \text{ A}, \quad t \geq 0^+ \\
[\text{c}] \quad 5 - 2.5e^{-500t} &= 3 \\
2 &= 2.5e^{-500t} \\
e^{500t} &= 1.25 \quad \therefore t = 446.29 \mu\text{s}
\end{aligned}$$

将左右分成两个独立的电路，当 $t=0$ 时，左侧电路对 i 的作用为 5 右侧电路为反向的 2.5


时间常数主要时观察放电过程中，哪些电阻对其有影响，电流只在右侧的环中，所以电阻为 25

注意：电阻中的电流可以瞬间变化


7.14 The switch in Fig. P7.14 has been closed for a long time before opening at $t = 0$. Find

- $i_L(t)$, $t \geq 0$.
- $v_L(t)$, $t \geq 0^+$.
- $i_\Delta(t)$, $t \geq 0^+$.

Figure P7.14

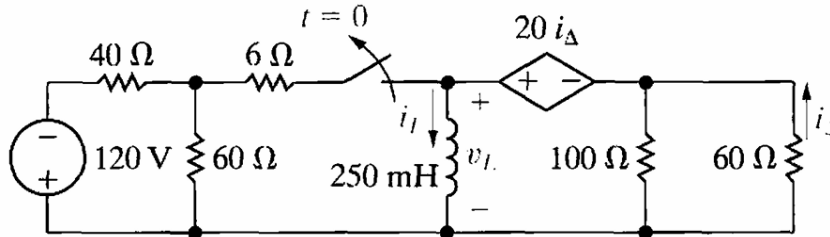


P 7.14 [a] $t < 0$:

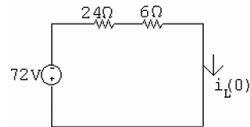

$$i_L(0) = -\frac{72}{24 + 6} = -2.4 \text{ A}$$


$t > 0$:

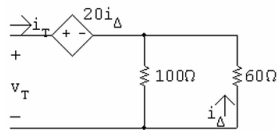

$$i_\Delta = -\frac{100}{160}i_T = -\frac{5}{8}i_T$$

$$v_T = 20i_\Delta + i_T \frac{(100)(60)}{160} = -12.5i_T + 37.5i_T$$
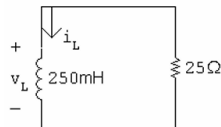
$$\frac{v_T}{i_T} = R_{Th} = -12.5 + 37.5 = 25 \Omega$$



$$\tau = \frac{L}{R} = \frac{250 \times 10^{-3}}{25} \quad \frac{1}{\tau} = 100$$

$$i_L = -2.4e^{-100t} \text{ A}, \quad t \geq 0$$

[b] $v_L = 250 \times 10^{-3}(240e^{-100t}) = 60e^{-100t} \text{ V}, \quad t \geq 0^+$

[c] $i_\Delta = 0.625i_L = -1.5e^{-100t} \text{ A} \quad t \geq 0^+$

7.15 What percentage of the initial energy stored in the inductor in the circuit in Fig. P7.14 is dissipated by the 60Ω resistor?

$$\text{P 7.15} \quad w(0) = \frac{1}{2}(250 \times 10^{-3})(-2.4)^2 = 720 \text{ mJ}$$

$$p_{60\Omega} = 60(-1.5e^{-100t})^2 = 135e^{-200t} \text{ W}$$


$$w_{60\Omega} = \int_0^\infty 135e^{-200t} dt = 135 \frac{e^{-200t}}{-200} \Big|_0^\infty = 675 \text{ mJ}$$

$$\% \text{ dissipated} = \frac{675}{720}(100) = 93.75\%$$

7.23 The switch in the circuit in Fig. P7.23 has been in position a for a long time and $v_2 = 0 \text{ V}$. At $t = 0$, the switch is thrown to position b. Calculate


- i , v_1 , and v_2 for $t \geq 0^+$.
- the energy stored in the capacitor at $t = 0$.
- the energy trapped in the circuit and the total energy dissipated in the $25 \text{ k}\Omega$ resistor if the switch remains in position b indefinitely.

Figure P7.23

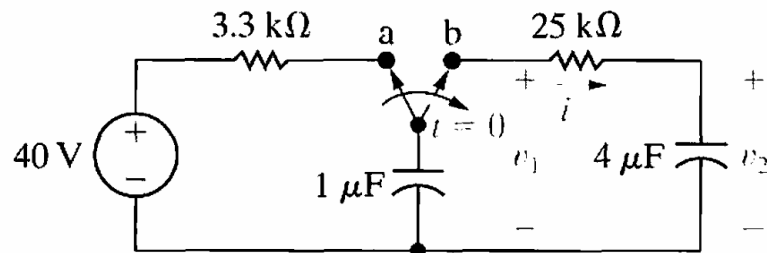


$$\text{P 7.23} \quad [\text{a}] \quad v_1(0^-) = v_1(0^+) = 40 \text{ V} \quad v_2(0^+) = 0$$
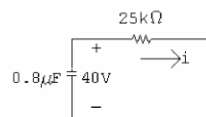
$$C_{\text{eq}} = (1)(4)/5 = 0.8 \mu\text{F}$$



$$\tau = (25 \times 10^3)(0.8 \times 10^{-6}) = 20 \text{ ms}; \quad \frac{1}{\tau} = 50$$
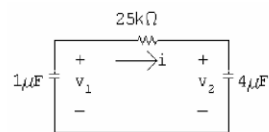
$$i = \frac{40}{25,000} e^{-50t} = 1.6e^{-50t} \text{ mA}, \quad t \geq 0^+$$



$$v_1 = \frac{-1}{10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 40 = 32e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

$$v_2 = \frac{1}{4 \times 10^{-6}} \int_0^t 1.6 \times 10^{-3} e^{-50x} dx + 0 = -8e^{-50t} + 8 \text{ V}, \quad t \geq 0$$

[b] $w(0) = \frac{1}{2}(10^{-6})(40)^2 = 800 \mu\text{J}$

[c] $w_{\text{trapped}} = \frac{1}{2}(10^{-6})(8)^2 + \frac{1}{2}(4 \times 10^{-6})(8)^2 = 160 \mu\text{J}.$

The energy dissipated by the 25 kΩ resistor is equal to the energy dissipated by the two capacitors; it is easier to calculate the energy dissipated by the capacitors:


$$w_{\text{diss}} = \frac{1}{2}(0.8 \times 10^{-6})(40)^2 = 640 \mu\text{J}.$$

Check: $w_{\text{trapped}} + w_{\text{diss}} = 160 + 640 = 800 \mu\text{J}; \quad w(0) = 800 \mu\text{J}.$

7.41 The switch in the circuit in Fig. P7.41 has been open a long time before closing at $t = 0$. Find $v_o(t)$ for $t \geq 0^+$.

PSPICE
MULTISIM

Figure P7.41

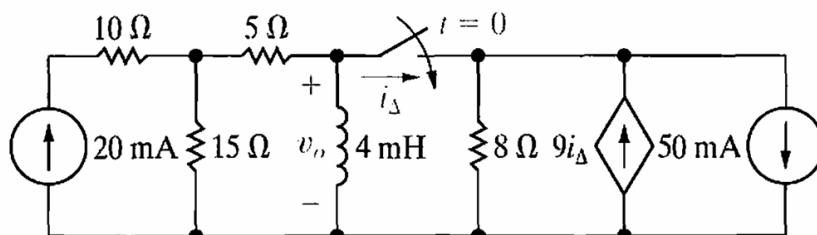


先对左右各进行一次戴维南等效，最后将左右两次一起等效成一个戴维南


PSPICE
MULTISIM

- 8.18** The two switches in the circuit seen in Fig. P8.18 operate synchronously. When switch 1 is in position a, switch 2 is in position d. When switch 1 moves to position b, switch 2 moves to position c. Switch 1 has been in position a for a long time. At $t = 0$, the switches move to their alternate positions. Find $v_o(t)$ for $t \geq 0$.


Figure P8.18

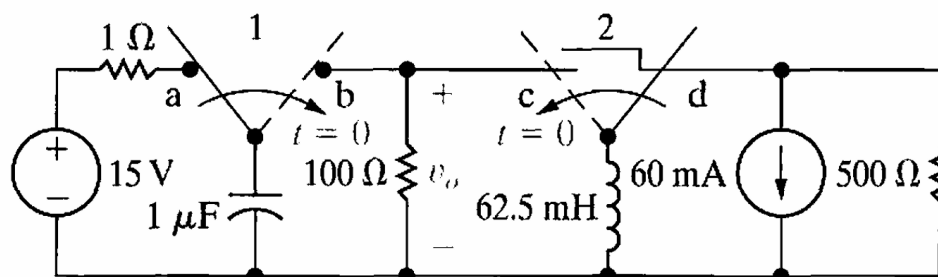

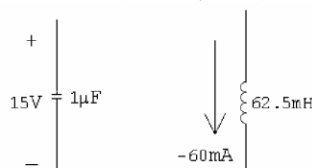P 8.18 $t < 0$: $V_o = 15\text{ V}$, $I_o = -60\text{ mA}$



$t > 0$:

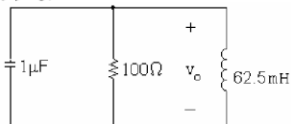

$$i_R(0) = \frac{15}{100} = 150\text{ mA}; \quad i_L(0) = -60\text{ mA}$$

$$i_C(0) = -150 - (-60) = -90\text{ mA}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2(100)(10^{-6})} = 5000\text{ rad/s}$$

$$\omega_o^2 = \frac{1}{LC} = \frac{1}{(62.5 \times 10^{-3})(10^{-6})} = 16 \times 10^6$$

$$s_{1,2} = -5000 \pm \sqrt{25 \times 10^6 - 16 \times 10^6} = -5000 \pm 3000$$

$$s_1 = -2000\text{ rad/s}; \quad s_2 = -8000\text{ rad/s}$$

$$\therefore v_o = A_1 e^{-2000t} + A_2 e^{-8000t}$$

$$A_1 + A_2 = v_o(0) = 15$$

$$\frac{dv_o}{dt}(0) = -2000A_1 - 8000A_2 = \frac{-90 \times 10^{-3}}{10^{-6}} = -90,000$$

$$\text{Solving, } A_1 = 5\text{ V}, \quad A_2 = 10\text{ V}$$

$$\therefore v_o = 5e^{-2000t} + 10e^{-8000t}\text{ V}, \quad t \geq 0$$

第一步：将电路化简到最简形式

第二步：判断是并联还是串联 RLC

第三步：计算衰减系数与谐振频率，判断是哪种类型的振荡

第四步：求出特征根


第五步：带出 0 时刻， $A_1 + A_2$ = 初始的电压或者电流

第六步：根据 KCL，列出等式（初始就有的电流之间带出，还有一个需要求一次导）

8.45 The switch in the circuit shown in Fig. P8.45 has been in position a for a long time. At $t = 0$, the switch is moved instantaneously to position b. Find $i(t)$ for $t \geq 0$.

PSpice
MULTISIM

Figure P8.45

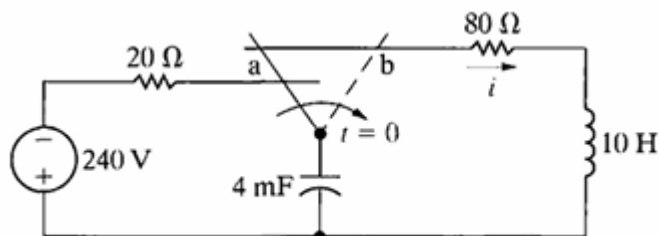

$$\text{P 8.45} \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(10)(4 \times 10^{-3})} = 25$$

$$\alpha = \frac{R}{2L} = \frac{80}{2(10)} = 4; \quad \alpha^2 = 16$$

$$\alpha^2 < \omega_o^2 \quad \therefore \quad \text{underdamped}$$

$$s_{1,2} = -4 \pm j\sqrt{9} = -4 \pm j3 \text{ rad/s}$$

$$i = B_1 e^{-4t} \cos 3t + B_2 e^{-4t} \sin 3t$$

$$i(0) = B_1 = -240/100 = -2.4 \text{ A}$$

$$\frac{di}{dt}(0) = 3B_2 - 4B_1 = 0$$

$$\therefore B_2 = -3.2 \text{ A}$$

$$i = -2.4e^{-4t} \cos 3t - 3.2 \sin 3t \text{ A}, \quad t \geq 0$$

8.46 The switch in the circuit in Fig. P8.46 on the next page has been in position a for a long time. At $t = 0$, the switch moves instantaneously to position b.


PSpice
MULTISIM

a) What is the initial value of v_a ?


b) What is the initial value of dv_a/dt ?

c) What is the numerical expression for $v_a(t)$ for $t \geq 0$?

Figure P8.46

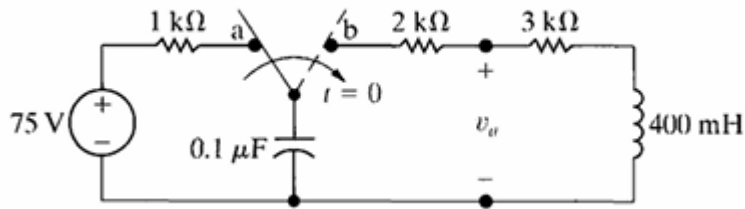

P 8.46 [a] For $t > 0$:

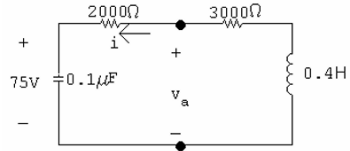

Since $i(0^-) = i(0^+) = 0$

$v_a(0^+) = 75 \text{ V}$

[b] $v_a = 2000i + 10^7 \int_0^t i \, dx + 75$

$$\frac{dv_a}{dt} = 2000 \frac{di}{dt} + 10^7 i$$

$$\frac{dv_a(0^+)}{dt} = 2000 \frac{di(0^+)}{dt} + 10^7 i(0^+) = 2000 \frac{di(0^+)}{dt}$$

$$-L \frac{di(0^+)}{dt} = 75$$

$$\frac{di(0^+)}{dt} = -2.5(75) = -187.5 \text{ A/s}$$

$$\therefore \frac{dv_a(0^+)}{dt} = -375,000 \text{ V/s}$$

[c] $\alpha = \frac{R}{2L} = \frac{5000}{0.8} = 6250 \text{ rad/s}$

$$\omega_o^2 = \frac{1}{LC} = \frac{10^6}{(0.4)(0.1)} = 25 \times 10^6$$

$$s_{1,2} = -6250 \pm \sqrt{6250^2 - 25 \times 10^6} = -6250 \pm 3750 \text{ rad/s}$$

$$\therefore s_1 = -2500 \text{ rad/s}; \quad s_2 = -10,000 \text{ rad/s}$$

Overdamped:

$$v_a = A_1 e^{-2500t} + A_2 e^{-10,000t}$$


$$v_a(0) = A_1 + A_2 = 75 \text{ V}$$

$$\frac{dv_a(0)}{dt} = -2500A_1 - 10,000A_2 = -375,000; \quad \therefore A_1 = 50 \text{ V}, \quad A_2 = 25 \text{ V}$$

$$v_a = 50e^{-2500t} + 25e^{-10,000t} \text{ V}, \quad t \geq 0^+$$

9.8 Find the rms value of the half-wave rectified sinusoidal voltage shown.

Figure P9.8

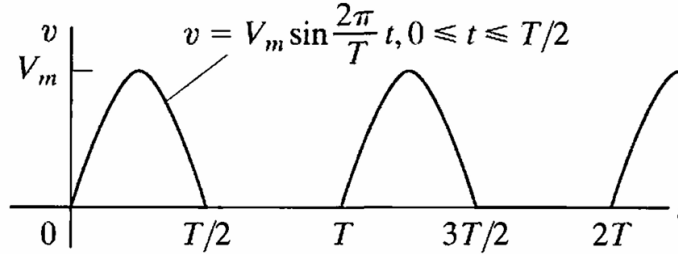

$$\text{P 9.8} \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \int_0^{T/2} V_m^2 \sin^2 \frac{2\pi}{T} t \, dt}$$

$$\int_0^{T/2} V_m^2 \sin^2 \left(\frac{2\pi}{T} t \right) dt = \frac{V_m^2}{2} \int_0^{T/2} \left(1 - \cos \frac{4\pi}{T} t \right) dt = \frac{V_m^2 T}{4}$$

$$\text{Therefore} \quad V_{\text{rms}} = \sqrt{\frac{1}{T} \frac{V_m^2 T}{4}} = \frac{V_m}{2}$$

9.9 The voltage applied to the circuit shown in Fig. 9.5 at $t = 0$ is $20 \cos(800t + 25^\circ)$ V. The circuit resistance is $80 \, \Omega$ and the initial current in the $75 \, \text{mH}$ inductor is zero.

- Find $i(t)$ for $t \geq 0$.
- Write the expressions for the transient and steady-state components of $i(t)$.
- Find the numerical value of i after the switch has been closed for $1.875 \, \text{ms}$.
- What are the maximum amplitude, frequency (in radians per second), and phase angle of the steady-state current?
- By how many degrees are the voltage and the steady-state current out of phase?

P 9.9 [a] The numerical values of the terms in Eq. 9.8 are

$$V_m = 20, \quad R/L = 1066.67, \quad \omega L = 60$$

$$\sqrt{R^2 + \omega^2 L^2} = 100$$

$$\phi = 25^\circ, \quad \theta = \tan^{-1} 60/80, \quad \theta = 36.87^\circ$$

Substitute these values into Equation 9.9:

$$i = [-195.72e^{-1066.67t} + 200 \cos(800t - 11.87^\circ)] \, \text{mA}, \quad t \geq 0$$

[b] Transient component = $-195.72e^{-1066.67t} \, \text{mA}$

$$\text{Steady-state component} = 200 \cos(800t - 11.87^\circ) \, \text{mA}$$

[c] By direct substitution into Eq 9.9 in part (a), $i(1.875 \, \text{ms}) = 28.39 \, \text{mA}$

[d] $200 \, \text{mA}$, $800 \, \text{rad/s}$, -11.87°

[e] The current lags the voltage by 36.87° .

注意 θ 的表达式, 是 $\theta = \arctan(\omega L/R)$

9.11 Use the concept of the phasor to combine the following sinusoidal functions into a single trigonometric expression:

a) $y = 50 \cos(500t + 60^\circ) + 100 \cos(500t - 30^\circ)$,

b) $y = 200 \cos(377t + 50^\circ) - 100 \sin(377t + 150^\circ)$,

P 9.11 [a] $\mathbf{Y} = 50/\underline{60^\circ} + 100/\underline{-30^\circ} = 111.8/\underline{-3.43^\circ}$

$$y = 111.8 \cos(500t - 3.43^\circ)$$

[b] $\mathbf{Y} = 200/\underline{50^\circ} - 100/\underline{60^\circ} = 102.99/\underline{40.29^\circ}$

$$y = 102.99 \cos(377t + 40.29^\circ)$$

[c] $\mathbf{Y} = 80/\underline{30^\circ} - 100/\underline{-225^\circ} + 50/\underline{-90^\circ} = 161.59/\underline{-29.96^\circ}$

$$y = 161.59 \cos(100t - 29.96^\circ)$$

先将 $\cos$ 进行相量转换, 然后在换成复数, 复数加减之后, 再写出对应的相量, 最后转回 $\cos$


9.12 The expressions for the steady-state voltage and current at the terminals of the circuit seen in Fig. P9.12 are

$$v_g = 300 \cos(5000\pi t + 78^\circ) \text{ V},$$

$$i_g = 6 \sin(5000\pi t + 123^\circ) \text{ A}$$

- a) What is the impedance seen by the source?
- b) By how many microseconds is the current out of phase with the voltage?

Figure P9.12

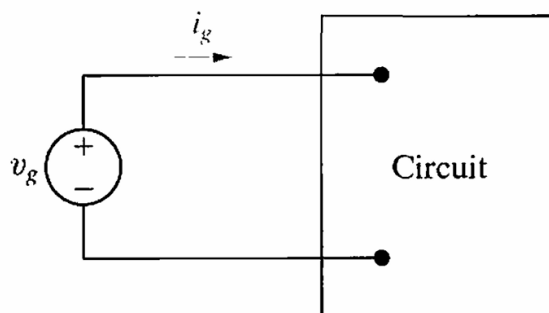

P 9.12 [a] $\mathbf{V}_g = 300\angle 78^\circ$; $\mathbf{I}_g = 6\angle 33^\circ$

$$\therefore Z = \frac{\mathbf{V}_g}{\mathbf{I}_g} = \frac{300\angle 78^\circ}{6\angle 33^\circ} = 50\angle 45^\circ \Omega$$

[b] i_g lags v_g by 45° :

$$2\pi f = 5000\pi; \quad f = 2500 \text{ Hz}; \quad T = 1/f = 400 \mu\text{s}$$


$$\therefore i_g \text{ lags } v_g \text{ by } \frac{45^\circ}{360^\circ}(400 \mu\text{s}) = 50 \mu\text{s}$$

阻抗直接使用相量来计算，不用再转会复数


10.24 The three loads in the circuit shown in Fig. P10.24 are $S_1 = 5 + j1.25$ kVA, $S_2 = 6.25 + j2.5$ kVA, and $S_3 = 8 + j0$ kVA.

- Calculate the complex power associated with each voltage source, $\mathbf{V}_{g1}$ and $\mathbf{V}_{g2}$.
- Verify that the total real and reactive power delivered by the sources equals the total real and reactive power absorbed by the network.

Figure P10.24

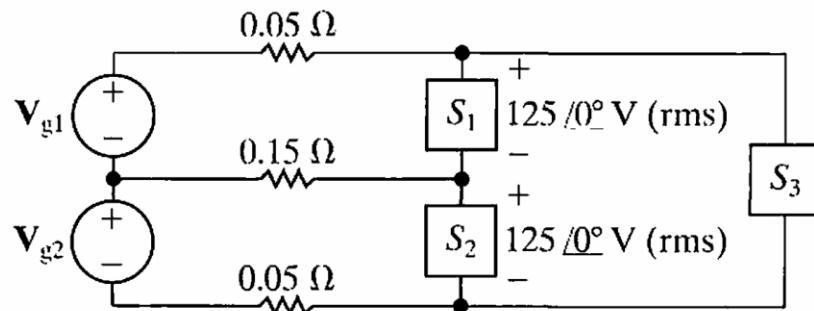

P 10.24 [a]

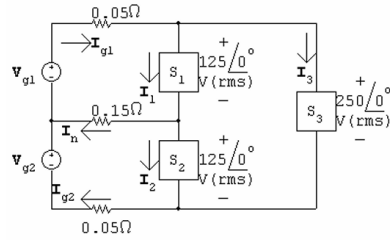

$$\mathbf{I}_1 = \frac{5000 - j1250}{125} = 40 - j10 \text{ A (rms)}$$

$$\mathbf{I}_2 = \frac{6250 - j2500}{125} = 50 - j20 \text{ A (rms)}$$

$$\mathbf{I}_3 = \frac{8000 + j0}{250} = 32 + j0 \text{ A (rms)}$$

$$\therefore \mathbf{I}_{g1} = 72 - j10 \text{ A (rms)}$$

$$\mathbf{I}_n = \mathbf{I}_1 - \mathbf{I}_2 = -10 + j10 \text{ A (rms)}$$

$$\mathbf{I}_{g2} = 82 - j20 \text{ A}$$

$$\mathbf{V}_{g1} = 0.05\mathbf{I}_{g1} + 125 + j0 + 0.15\mathbf{I}_n = 127.1 - j1 \text{ V(rms)}$$

$$\mathbf{V}_{g2} = -0.15\mathbf{I}_n + 125 + j0 + 0.05\mathbf{I}_{g2} = 130.6 - j2.5 \text{ V(rms)}$$

$$S_{g1} = -[(127.1 - j1)(72 + j10)] = -[9141.2 + j1343] \text{ VA}$$

$$S_{g2} = -[(130.6 - j2.5)(82 + j20)] = -[10,759.2 + j2407] \text{ VA}$$

Note: Both sources are delivering average power and magnetizing VAR to the circuit.

$$[b] P_{0.05} = |\mathbf{I}_{g1}|^2(0.05) = 264.2 \text{ W}$$

$$P_{0.15} = |\mathbf{I}_n|^2(0.15) = 30 \text{ W}$$

$$P_{0.05} = |\mathbf{I}_{g2}|^2(0.05) = 356.2 \text{ W}$$

$$\sum P_{\text{dis}} = 264.2 + 30 + 356.2 + 5000 + 8000 + 6250 = 19,900.4 \text{ W}$$

$$\sum P_{\text{dev}} = 9141.2 + 10,759.2 = 19,900.4 \text{ W} = \sum P_{\text{dis}}$$

$$\sum Q_{\text{abs}} = 1250 + 2500 = 3750 \text{ VAR}$$


$$\sum Q_{\text{del}} = 1343 + 2407 = 3750 \text{ VAR} = \sum Q_{\text{abs}}$$

注意有些地方要使用共轭。正常计算 $\mathbf{I}^* = \mathbf{S}/\mathbf{V}$


10.50 The variable resistor R_o in the circuit shown in Fig. P10.50 is adjusted until maximum average power is delivered to R_o .

- What is the value of R_o in ohms?
- Calculate the average power delivered to R_o .
- If R_o is replaced with a variable impedance Z_o , what is the maximum average power that can be delivered to Z_o ?
- In (c), what percentage of the circuit's developed power is delivered to the load Z_o ?

Figure P10.50

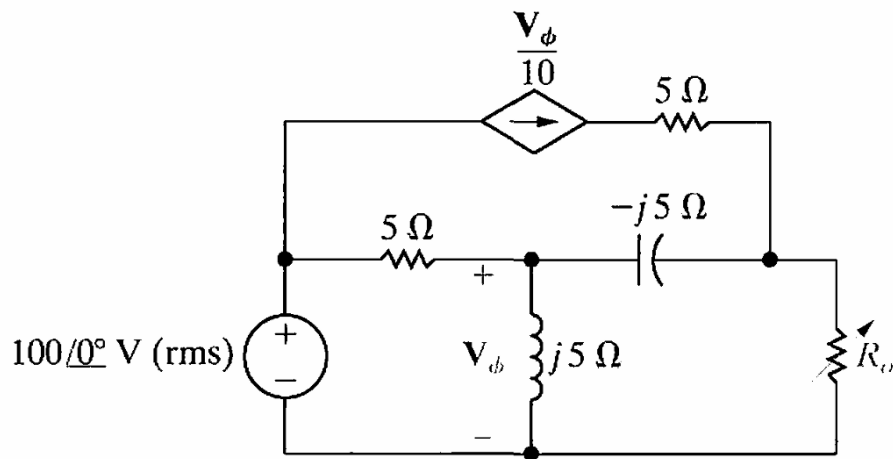

[d]

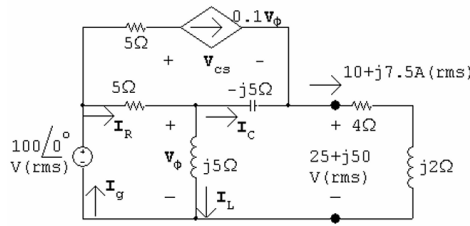

$$\frac{V_\phi - 100}{5} + \frac{V_\phi}{j5} + \frac{V_o - (25 + j50)}{-j5} = 0$$

$$V_\phi = 50 + j25 \text{ V (rms)}$$

$$0.1V_\phi = 5 + j2.5 \text{ V (rms)}$$

$$5 + j2.5 + I_C = 10 + j7.5$$

$$I_C = 5 + j5 \text{ A (rms)}$$

$$I_L = \frac{V_\phi}{j5} = 5 - j10 \text{ A (rms)}$$

$$I_R = I_C + I_L = 10 - j5 \text{ A (rms)}$$

$$I_g = I_R + 0.1V_\phi = 15 - j2.5 \text{ A (rms)}$$

$$S_g = -100I_g^* = -1500 - j250 \text{ VA}$$

$$100 = 5(5 + j2.5) + V_{cs} + 25 + j50 \quad \therefore \quad V_{cs} = 50 - j62.5 \text{ V (rms)}$$

$$S_{cs} = (50 - j62.5)(5 - j2.5) = 93.75 - j437.5 \text{ VA}$$

Thus,

$$\sum P_{\text{dev}} = 1500$$

$$\% \text{ delivered to } R_o = \frac{625}{1500}(100) = 41.67\%$$

注意，受控电流源是在消耗功率

12.25 Find the Laplace transform for (a) and (b).

a) $f(t) = \frac{d}{dt}(e^{-at} \sin \omega t).$

b) $f(t) = \int_{0^-}^t e^{-ax} \cos \omega x \, dx.$

c) Verify the results obtained in (a) and (b) by first carrying out the indicated mathematical operation and then finding the Laplace transform.

P 12.25 [a] $f_1(t) = e^{-at} \sin \omega t$; $F_1(s) = \frac{\omega}{(s+a)^2 + \omega^2}$

$$F(s) = sF_1(s) - f_1(0^-) = \frac{s\omega}{(s+a)^2 + \omega^2} - 0$$

[b] $f_1(t) = e^{-at} \cos \omega t$; $F_1(s) = \frac{s+a}{(s+a)^2 + \omega^2}$

$$F(s) = \frac{F_1(s)}{s} = \frac{s+a}{s[(s+a)^2 + \omega^2]}$$

[c] $\frac{d}{dt}[e^{-at} \sin \omega t] = \omega e^{-at} \cos \omega t - a e^{-at} \sin \omega t$

$$\text{Therefore } F(s) = \frac{\omega(s+a) - \omega a}{(s+a)^2 + \omega^2} = \frac{\omega s}{(s+a)^2 + \omega^2}$$

$$\int_{0^-}^t e^{-ax} \cos \omega x dx = \frac{-a e^{-at} \cos \omega t + \omega e^{-at} \sin \omega t + a}{a^2 + \omega^2}$$


Therefore

$$\begin{aligned} F(s) &= \frac{1}{a^2 + \omega^2} \left[\frac{-a(s+a)}{(s+a)^2 + \omega^2} + \frac{\omega^2}{(s+a)^2 + \omega^2} + \frac{a}{s} \right] \\ &= \frac{s+a}{s[(s+a)^2 + \omega^2]} \end{aligned}$$

14.25 For the bandpass filter shown in Fig. P14.25, calculate the following: (a) f_o ; (b) Q ; (c) f_{c1} ; (d) f_{c2} ; and (e) β .

PSPICE
MULTISIM

Figure P14.25

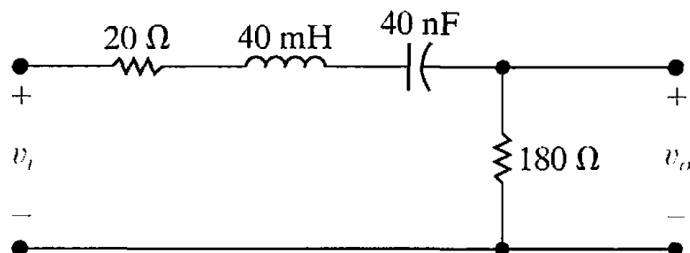

$$\text{P 14.25 [a]} \quad \omega_o^2 = \frac{1}{LC} = \frac{1}{(40 \times 10^{-3})(40 \times 10^{-9})} = 625 \times 10^6$$

$$\omega_o = 25 \times 10^3 \text{ rad/s} = 25 \text{ krad/s}$$

$$f_o = \frac{25,000}{2\pi} = 3978.87 \text{ Hz}$$

$$\text{[b]} \quad Q = \frac{\omega_o L}{R + R_i} = \frac{(25 \times 10^3)(40 \times 10^{-3})}{200} = 5$$

$$\begin{aligned} \text{[c]} \quad \omega_{c1} &= \omega_o \left[-\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right] = 25,000 \left[-\frac{1}{10} + \sqrt{1 + \frac{1}{100}} \right] \\ &= 22.62 \text{ krad/s} \quad \text{or} \quad 3.60 \text{ kHz} \end{aligned}$$

$$\begin{aligned} \text{[d]} \quad \omega_{c2} &= \omega_o \left[\frac{1}{2Q} + \sqrt{1 + \left(\frac{1}{2Q}\right)^2} \right] = 25,000 \left[\frac{1}{10} + \sqrt{1 + \frac{1}{100}} \right] \\ &= 27.62 \text{ krad/s} \quad \text{or} \quad 4.4 \text{ kHz} \end{aligned}$$

$$\text{[e]} \quad \beta = \omega_{c2} - \omega_{c1} = 27.62 - 22.62 = 5 \text{ krad/s}$$

or

$$\beta = \frac{\omega_o}{Q} = \frac{25,000}{5} = 5 \text{ krad/s} \quad \text{or} \quad 795.77 \text{ Hz}$$

特别注意 β 的算法